

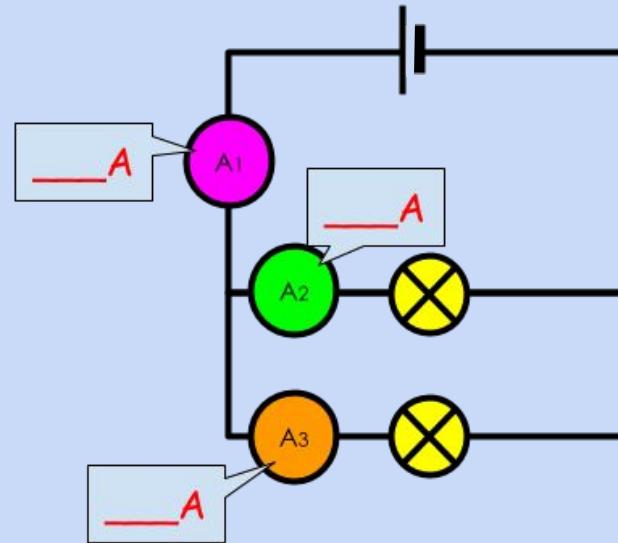


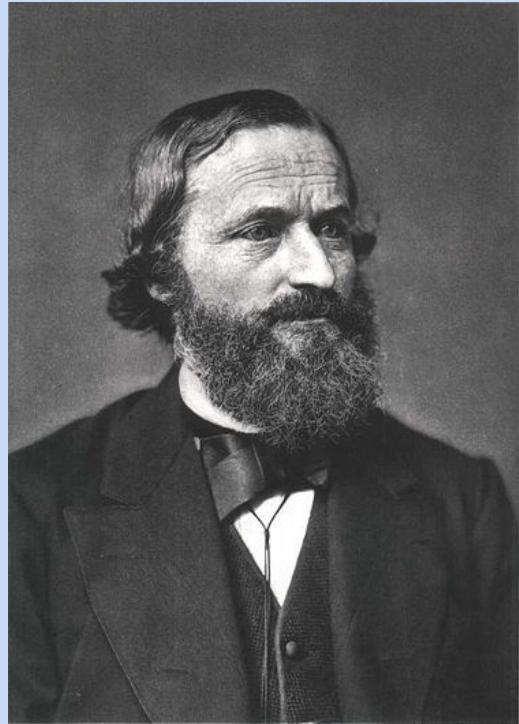
Ben's Research Lesson: what's the best way to teach Kirchoff's 1st Law?



I do

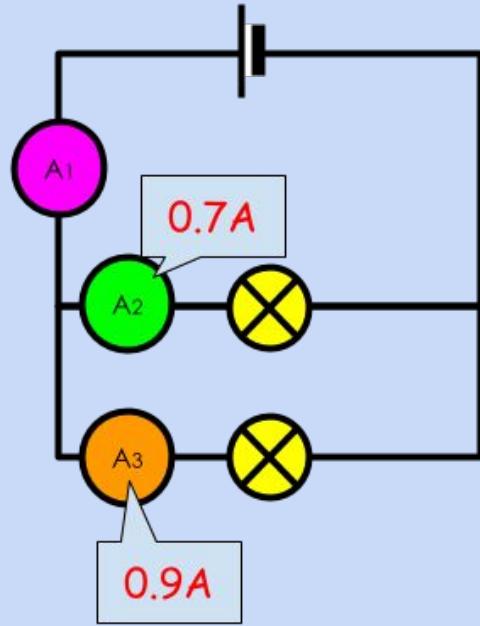


I do

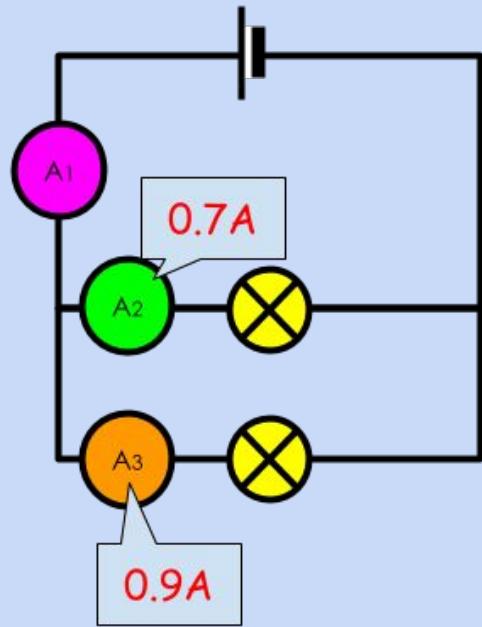

$$A_1 = A_2 + A_3$$


I do

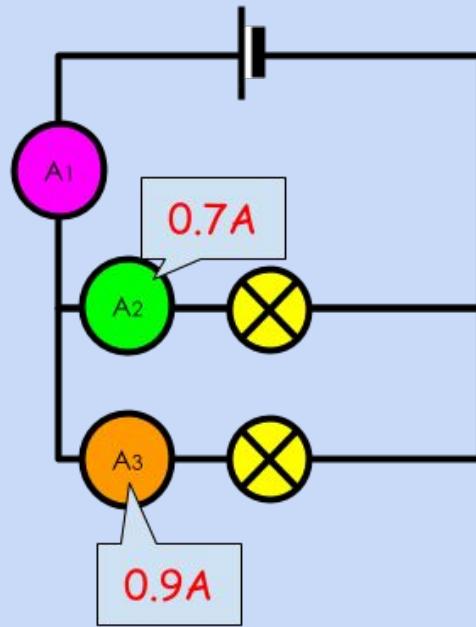

$$A_1 = A_2 + A_3$$

$$A = 0.7A + 0.9A$$

I do

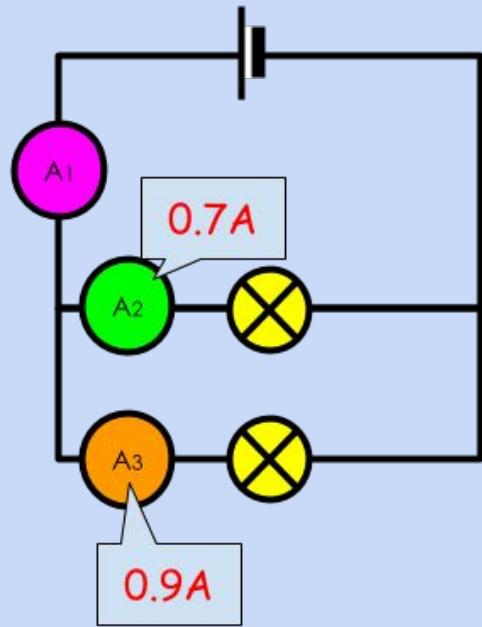


$$A_1 = A_2 + A_3$$

$$1.6A = 0.7A + 0.9A$$

I do

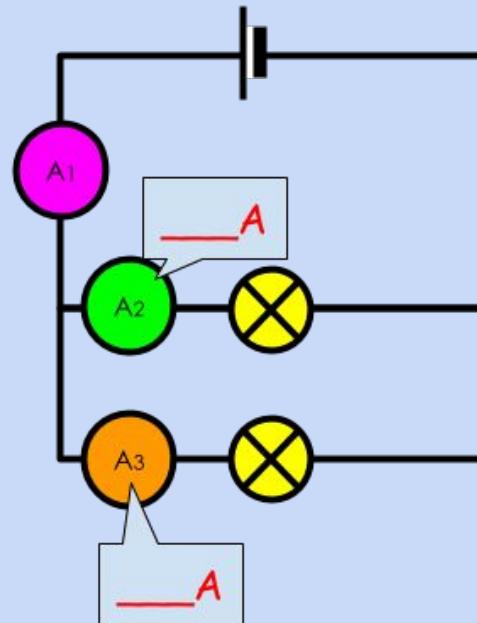
If the current through A_2 is 0.5A and the current through A_3 is 0.6A, what is the current through A_1 ?



I do

If the current through A_2 is 0.5A and the current through A_3 is 0.6A, what is the current through A_1 ?

$$A_1 = A_2 + A_3$$

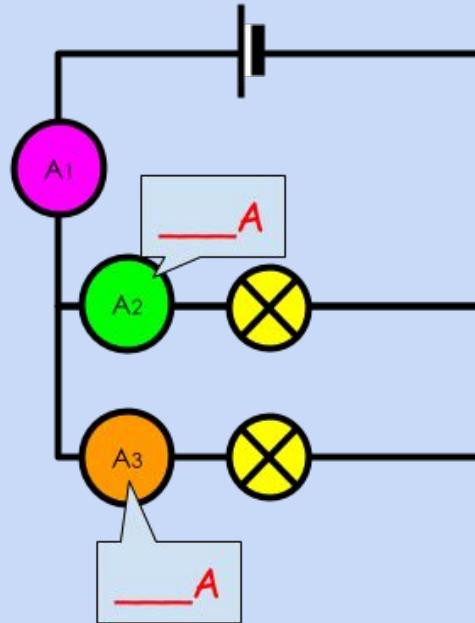


I do

If the current through A_2 is 0.5A and the current through A_3 is 0.6A, what is the current through A_1 ?


$$A_1 = A_2 + A_3$$

$$A = 0.5A + 0.6A$$

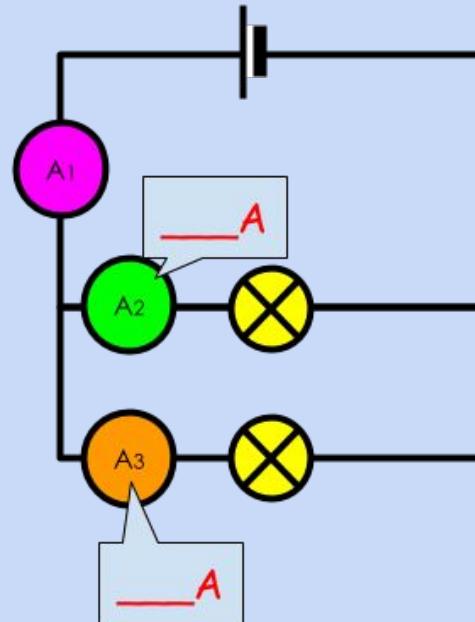

we
do

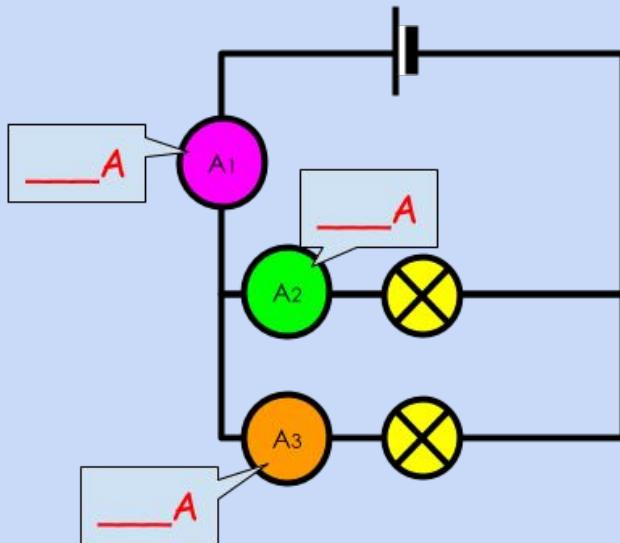If the current through A_2 is 1.2A and the current through A_3 is 0.8A, what is the current through A_1 ?




$$A_1 = A_2 + A_3$$

$$A = A + A$$

you
do

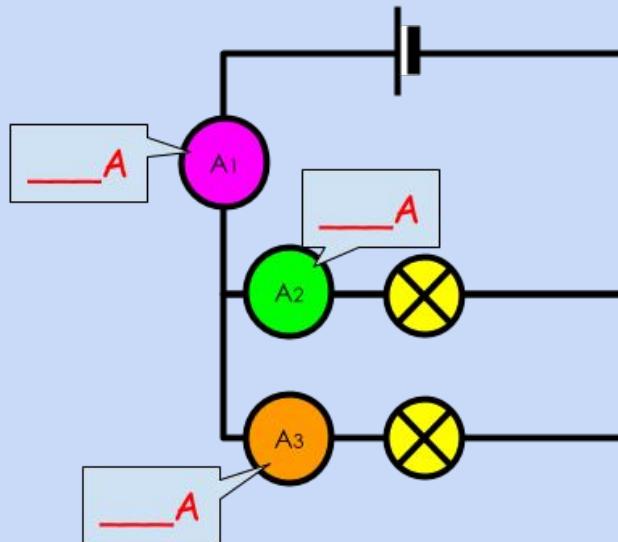If the current through A_2 is 1.0A and the current through A_3 is 0.9A, what is the current through A_1 ?




$$A_1 = A_2 + A_3$$

$$A = A + A$$

you
do

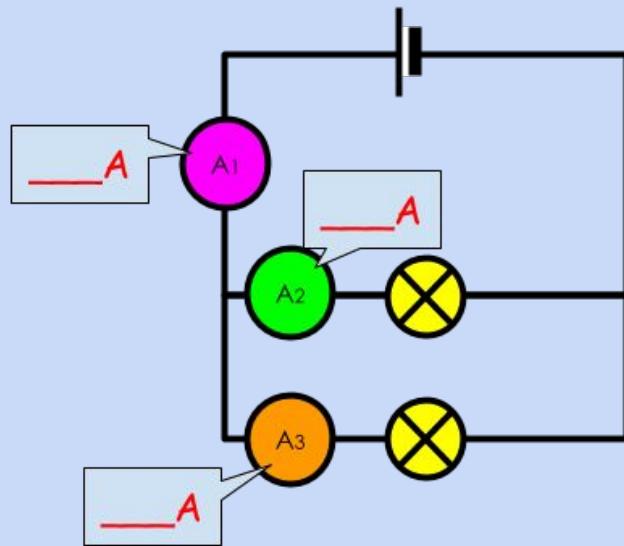If the current through A_1 is 1.8A and the current through A_2 is 0.9A, what is the current through A_3 ?



$$A_1 = A_2 + A_3$$

$$A = A + A$$

you
do

If the current through A_2 is 1.5A and the current through A_3 is 0.3A, what is the current through A_1 ?

